




ELC4005: Selected Topics in Electronics I

EECS331: Advanced Topics in Electronics I

Lecture 5

Low Noise Amplifiers

LNA Figure of Merit

 




- LNA should have a low NF along with adequate gain to suppress the noise of the subsequent Rx stages
- LNA figure of merit, defined by the ITRS roadmap:

$$FOM_{LNA} = \frac{G \times IIP_3 \times f}{(F - 1) \times P}$$

- Maximizing the FoM of the LNA implies simultaneously:
 - minimizing the noise factor
 - increasing the gain
 - maximizing linearity
 - minimizing power dissipation
 - reducing the input reflection coefficient

LOW-NOISE DESIGN PHILOSOPHY



Discrete
LNAs

   

MMICs

- **Traditional LNA design (before monolithic microwave integrated circuits MMICs) :**
 - Used **external** passive matching networks to transform Z_s to Z_{OPT} of a discrete transistor
 - **Discrete** transistor was biased at J_{OPT} (minimum NF_{min})
 - In general, $\text{Re}\{Z_{OPT}\}$ and $\text{Re}\{Z_{in}\}$ of the transistor are not equal \rightarrow sub-optimal S_{11} and gain for the LNA in order to minimize its noise factor
 - Measured S-parameters of the transistor at the J_{OPT} & the noise circles were used for design
- **Move to MMICs:**
 - integrated matching circuits & more flexibility in transistor sizing & biasing
 - On-chip lossy passive matching components \rightarrow New design methodology to reduce number/loss of passives **“Active matching”**

CS/CE with/without Cascode LNAs

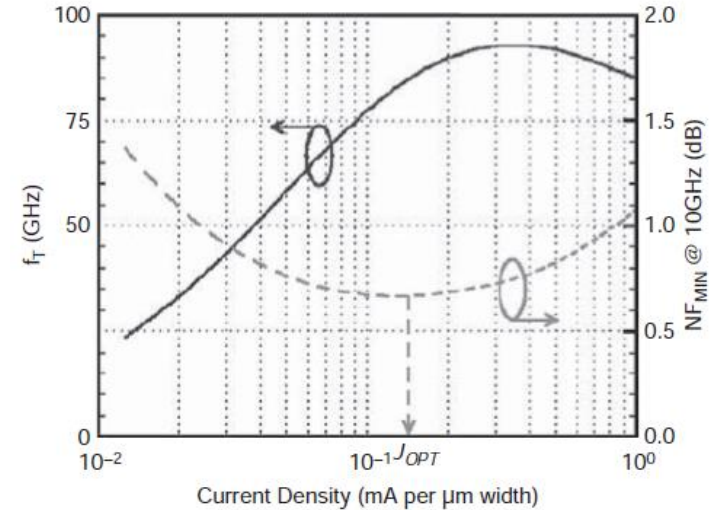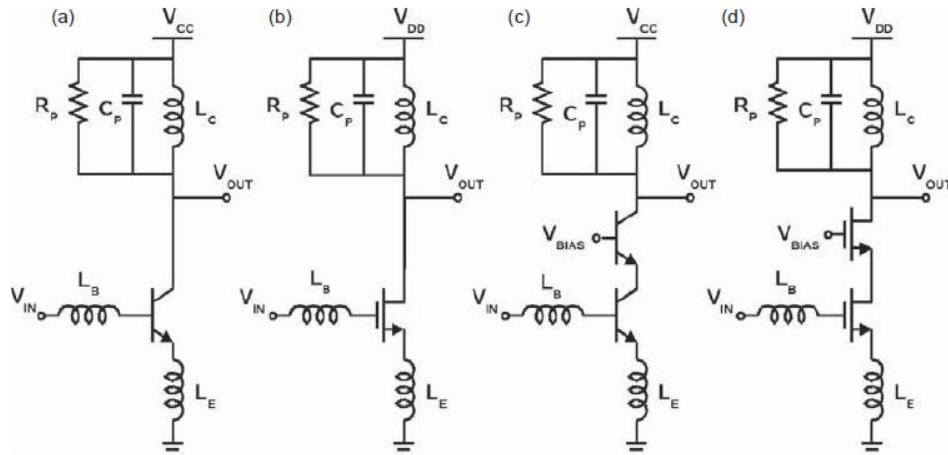

- CS/CE topologies are the most widely used LNAs → best NF & permit **simultaneous noise and input impedance matching**
- Cascode isolates output from input → extends BW & higher gain with low NF penalty
- Avoid active loads → increase noise & degrade linearity
- Fix transistor finger width W_f to get the desired R_g/F_{MAX}
- Sweep J_{DS} by changing the I_{DS} (or number of fingers N , $W = N \times W_f$)
- Bias the transistors at the J_{OPT} of the topology → lowest NF_{MIN}

CS LNAs: Active Noise Matching


$$J_{OPT} = \frac{I_{DS}}{W}$$

$$g_m = \sqrt{2\mu C_{OX} \frac{W}{L} I_{DS}} = W \sqrt{2\mu C_{OX} \frac{J_{OPT}}{L}}$$

$$Z_{SOPT}(FET) \approx \frac{1}{\omega(C_{gs} + C_{gd})} \left[\sqrt{\frac{g_m(R_s + R_g)}{k_1}} + j \right]$$

→ $re\{Z_{SOPT}\} \downarrow \text{ as } W \uparrow$

 - To minimize the number of components/simplify matching circuit → Active matching
- $Re\{Z_{SOPT}\}$ decreases as the total transistor W increases
- Calculate the total width W or (N) for optimum noise impedance, i.e. $re\{Z_{SOPT}\}=Z_o$
- Noise matching now only requires a single series reactive component → significant simplification to matching circuit



CS LNAs: Input Matching by Degeneration

- Adding a lossless degeneration inductor L_S forms a series-series feedback network
 - Doesn't change the $\text{re}\{Z_{\text{SOPT}}\}$
 - NF_{min} remains the same
 - Increases $\text{re}\{Z_{\text{in}}\}$ according to the following:


$$Z_{IN} \approx R_b + r_E + \omega_T L_E + j \left(\omega L_E + \omega L_B - \frac{1}{\omega C_{IN}} \right)$$

$$\Re\{Z_{IN, \text{MOS}}\} = R_g + r_s + R_{LB} + R_{LE} + \omega_T L_E$$

$$L_S = \frac{Z_0 - R_g - R_s}{2\pi f_T}$$


$$C_{IN} = C_{gseff} + C_{gd}$$

$$C_{IN} = \frac{g_{meff}}{\omega_T}$$

 


- Input of the LNA behaves as a series resonant RLC circuit
- $\text{Re}\{Z_{\text{in}}\}$ is freq. independent, proper choice of L_S can set $\text{Re}\{Z_{\text{in}}\} = Z_0$
- Only a single series reactive component is necessary to achieve input match \rightarrow simplify input matching/reduce its losses

Unilateral Transistor equivalent circuit

 

- Simplified, unilateral, transistor equivalent circuit based on frequency-dependent current source neglects feedback from output to input due to C_{gd}
- Model neglects Miller effect

Tuned CS LNA Gain

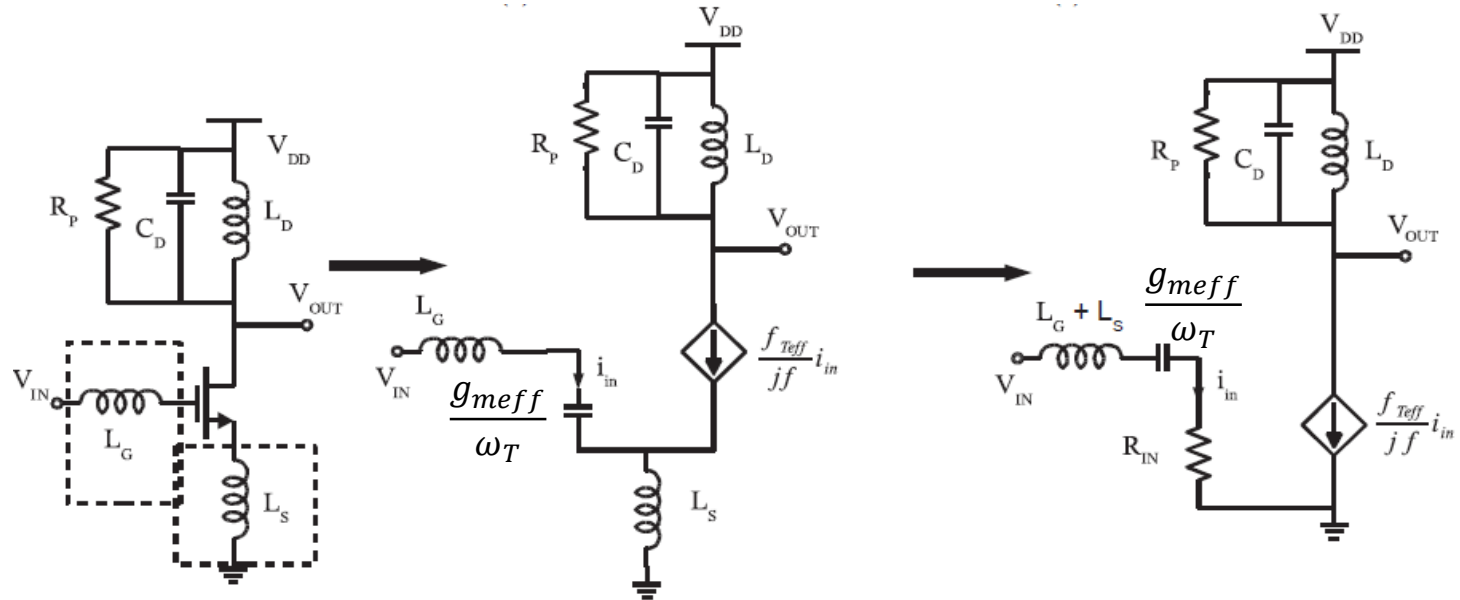

- Using the unilateral transistor equivalent circuit model

$$v_{in} = i_{in} \left(j\omega L_G + R_g + R_s + \frac{\omega T_{eff}}{j\omega g_{meff}} + j\omega L_S \right) + j\omega L_S \frac{\omega T_{eff}}{j\omega} i_{in} \quad i_{sc} = \frac{-f_{Teff}}{jf} i_{in} = j \frac{f_{Teff}}{f} i_{in}$$

$$Z_{in} = R_g + R_s + \omega T_{eff} L_S + j \left[\omega (L_G + L_S) - \frac{\omega T_{eff}}{\omega g_{meff}} \right] \quad C_{IN} = \frac{g_{meff}}{\omega T_{eff}} \text{ and } R_{IN} = R_s + R_g + \omega T_{eff} \times L_S$$

CS LNAs: Input Matching by Degeneration

- Adding a lossless degeneration inductor L_S forms a series-series feedback network
 - Doesn't change the $\text{re}\{Z_{\text{SOPT}}\}$
 - NF_{min} remains the same
 - Increases $\text{re}\{Z_{\text{in}}\}$ according to the following:


$$Z_{IN} \approx R_b + r_E + \omega_T L_E + j \left(\omega L_E + \omega L_B - \frac{1}{\omega C_{IN}} \right)$$

$$C_{IN} = \frac{g_{m\text{eff}}}{\omega_T}$$

$$\Re\{Z_{IN, \text{MOS}}\} = R_g + r_s + R_{LB} + R_{LE} + \omega_T L_E$$

$$C_{IN} = C_{g\text{seff}} + C_{gd}$$
 
$$L_S = \frac{Z_0 - R_g - R_s}{2\pi f_T}$$



- Input of the LNA behaves as a series resonant RLC circuit
- $\text{Re}\{Z_{\text{in}}\}$ is freq. independent, proper choice of L_S can set $\text{Re}\{Z_{\text{in}}\} = Z_0$
- Only a single series reactive component is necessary to achieve input match \rightarrow simplify input matching/reduce its losses


CS LNAs: Reactive Input/Noise Matching

$$Z_{IN} \approx R_b + r_E + \omega_T L_E + j \left(\omega L_E + \omega L_B - \frac{1}{\omega C_{IN}} \right)$$


- The input series inductor L_G is added to tune out the $\text{im}\{Z_{in}\}$ to zero at the LNA operating frequency:

$$L_G \approx \frac{\omega_T}{\omega^2 g_{m\text{eff}}} - L_S$$

 - For both FETs and HBTs, the imaginary part of the optimum noise impedance $\text{im}\{Z_{\text{SOPT}}\}$ and imaginary part of the input impedance $\text{im}\{Z_{in}\}$ are roughly equal
- L_G also cancels out $X_{\text{SOPT}} \rightarrow$ Simultaneous gain and noise match



Output matching to maximize gain

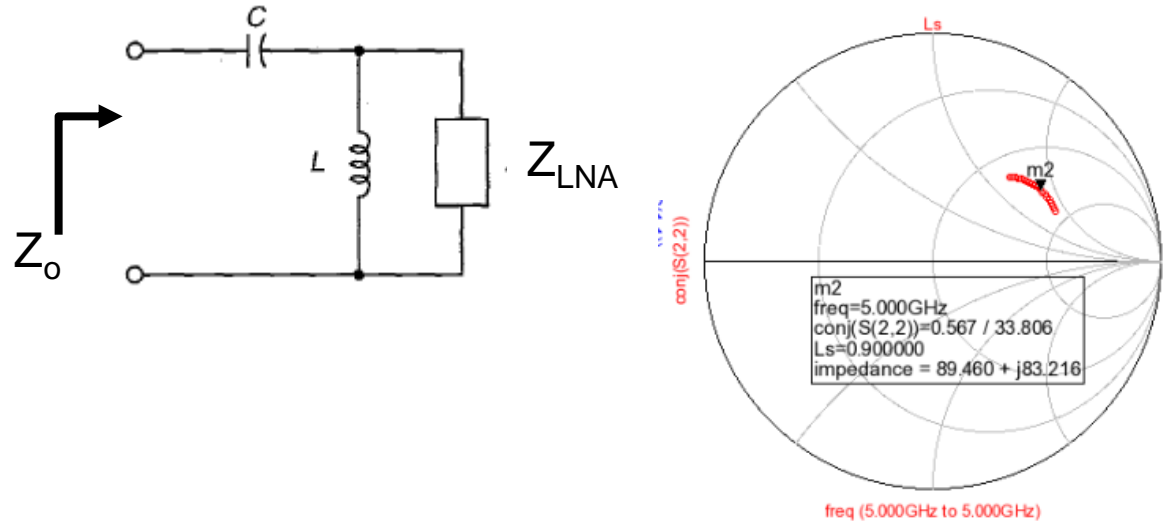

- LNA output impedance is usually capacitive with real part $> Z_o$
- The simplest matching network can be realized with an L-section
- A shunt inductor, L connected to VDD, followed by a series capacitor towards the load

Tuned CS LNA Gain (Cont'd)


$$V_{out} = \frac{I_{sc} \times R_P}{2} = j \frac{f_{Teff} \times R_P}{2f} i_{in}$$

$$I_{load} = \frac{I_{sc}}{2} = j \frac{f_{Teff}}{2f} i_{in}$$

$$P_{load} = V_{out} \times I_{load}^* = \frac{f_{Teff}^2 \times R_P}{4f^2} |i_{in}|^2$$

$$P_{in} = v_{in} \times i_{in}^* = i_{in} \times R_{IN} \times i_{in}^* = R_{IN} |i_{in}|^2.$$
 
$$i_{sc} = \frac{-f_{Teff}}{jf} i_{in} = j \frac{f_{Teff}}{f} i_{in}$$



- Only half of the short-circuit current ends up in the matched load, with the other half flowing through the R_P
- The power gain in a matched load R_P can be expressed:

$$G = \frac{P_{load}}{P_{in}} = \frac{f_{Teff}^2}{4f^2} \times \frac{R_P}{R_{IN}} \rightarrow R_{IN} = Z_0 \text{ for input matching}$$

- To maximize the LNA gain the parallel tank resistance R_P must be increased, i.e. designing for a high-Q load inductor L_D (narrowband)

$$R_P = Q\omega_0 L_C$$

CS/CE LNA Linearity

- Linearity is determined by the VGS non-linearity at large input voltages
- Series-Series feedback via L_S improves the LNA linearity by reducing the swing on VGS
- The linearity is proportional to the feedback provided by the L_S :

$$1 + j\omega L_S g_{m\text{eff}}$$

- To maximize linearity, the LNA transistor must be biased at high current density, (large g_m) & use a large L_S
- To increase LNA linearity:
 - Increase the bias current by making transistors larger while still biasing them at J_{OPT}
 - $R_{\text{SOPT}} < Z_o \rightarrow$ Noise impedance mismatch
 - R_n is reduced \rightarrow noise impedance mismatch does not lead to significant degradation from NF_{MIN}


$$F = F_{\text{MIN}} + \frac{R_n}{G_s} |Y_s - Y_{\text{sopt}}|^2$$

BW Extension for Cascode CS LNAs

- Cascode LNA allows increasing the LNA gain with slight hit in NF
- Cascode noise circulates in device
- Placing a shunt inductor L_{M1} to an AC ground \rightarrow resonates the parasitic capacitances:

$$C_{gd1} + C_{db1} + C_{sb2} + C_{gs2}$$

 - Shunt inductor \rightarrow narrow band resonance



- Series inductor L_{M1} forms an artificial transmission line
- This absorbs the effect of the parasitic capacitance
- L_{M1} also improves the noise figure of the cascode stage at mm-waves (CG noise sources degenerated by higher impedance)

BW Extension for Cascode CS LNAs

- The characteristic impedance of this TL can be expressed as:


$$Z_{01} = \sqrt{\frac{L_{M1}}{C_{gs2} + C_{sb2}}}$$

- The inductance L_{M1} is set to match the TL characteristic impedance to the impedance seen at the source of the CG:

$$Z_{01} = Z_{M2, in} = \frac{1}{g_{m2}} + \frac{\omega L_{D1} Q}{2(1 + g_{m2} r_{o2})}$$

Load impedance
at resonance

 - Satisfying this condition guarantees maximizing the cascode gain by avoiding interstage mismatches
- The 1/2 factor is due to the extra loading with a matched Z_L to that of the inductor L_{D1} at resonance




POWER-CONSTRAINED CMOS LNAs

- Drawback of CS LNA is the need for large device sizes (& I_{DS}) at frequencies below 20GHz \rightarrow higher power consumption
- Capacitor C_1 allows reducing R_{SOPT} until it reaches Z_0 **without increasing the LNA current:**

$$Z_{SOPT}(FET) \approx \frac{1}{\omega(C_{gs} + C_{gd})} \left[\sqrt{\frac{g_m(R_s + R_g)}{k_1}} + j \right]$$


$$\omega_T = \frac{g_m}{C_{gs} + 2C_{gd}}$$
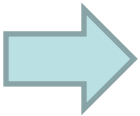
$$L_S = \frac{Z_0 - R_g - R_s}{2\pi f_T}$$




$$f'_T \rightarrow \frac{f_T}{1 + \frac{C_1}{C_{gs} + 2C_{gd}}}$$
 
$$L'_S \rightarrow L_S \left(1 + \frac{C_1}{C_{gs} + 2C_{gd}} \right)$$



- Drawbacks:
 - f_T of artificial transistor drops by $1 + C_1/(C_{gs} + 2C_{gd})$
 - Degeneration inductor increases by the same factor
 - LNA gain & NF_{MIN} will also degrade

LOW-VOLTAGE LNA TOPOLOGIES

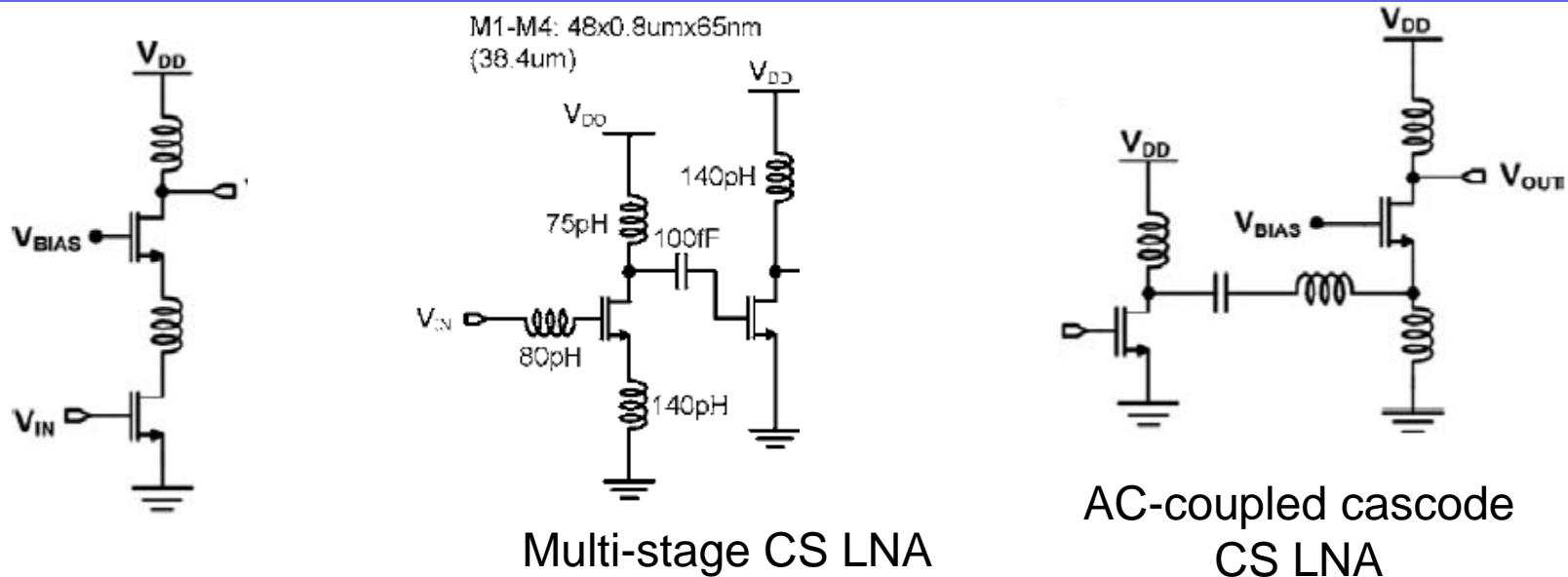


- In advanced CMOS nodes, supply voltages are reduced → can't stack FETs without reducing V_{DS} (degraded f_T and f_{MAX})
- Could employ a multi-stage CS LNA → degraded isolation
- AC-coupled cascode CS stages:
 - reduce the number of transistors in the vertical stack
 - robustness to process & supply variation
 - cost is doubling the bias current

Common Gate CG LNAs

- CG LNA are suitable for:
 - lower power LNAs
 - Wide bandwidth LNA down to DC
- Provides higher NF & lower linearity compared to CS/cascode LNAs
- The $\Re\{Z_{in}\}$ is set by I_{DS} (or g_m) of the transistor:

$$\Re\{Z_{IN,CG}\} = \frac{1}{g_{m,MOS}} + \frac{R_P}{1 + \frac{g_{m,MOS}}{g_o}}$$

 - Conductance g_o degrades the isolation input to output
- $\Re\{Z_{in}\}$ is a function of the bias and the load resistance (R_P)
- Input capacitance (C_{gs}) is canceled by the shunt inductor L_E
- To increase CG linearity higher current is required → trade-off between linearity and match
- **CG LNA can't be independently noise & impedance matched** (no independent parameters are available)





DIFFERENTIAL LNA DESIGNS

$$Z_{soptdiff} = 2Z_{sopt}(half_ckt)$$


$$Z_{INdiff} = 2\omega_T L_{S1}$$

  Common mode inductor
added to improve high
frequency CMRR




- The differential-mode Z_{SOPT} is 2x the differential-mode half circuit
- L_{S1} is the degeneration inductance per side and ω_T is the cutoff frequency of the differential-mode half circuit
- RF amplifiers typically don't use current sources for biasing due to their low CMRR at high frequency

LOW-NOISE BIAS NETWORKS FOR LNAs

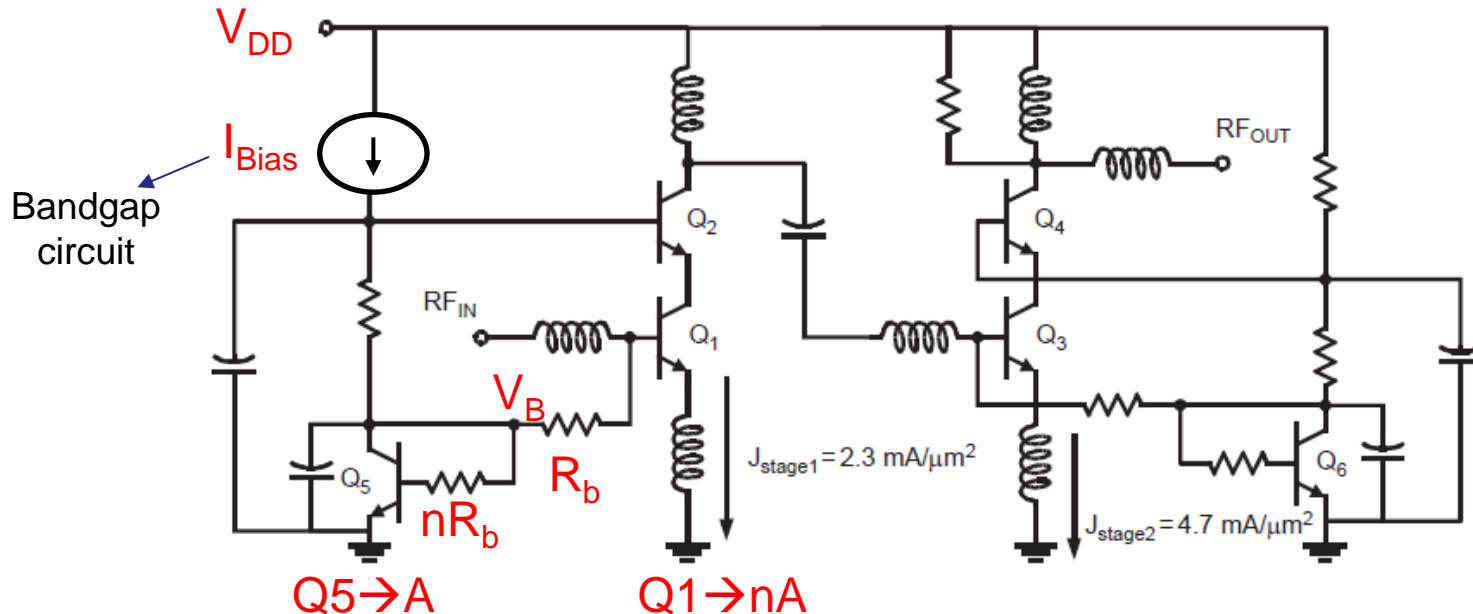

- Bias network must not degrade the NF, high resistance value for $R_b \sim 1\text{-}5\text{K}\Omega$ (R_b noise current $4kT/R$ input referred)
- Capacitors, are placed at the cascode base
 - Provides low impedance for gain improvement (gain vs. linearity trade-off)
 - Cascode base capacitor self-resonance frequency $>$ the highest frequency of interest to avoid oscillation
- Decoupling caps are placed at V_B (& V_{DD}) to provide a low impedance in the bandwidth of interest \rightarrow helps filter noise of bias circuit & supply


LOW-NOISE BIAS NETWORKS FOR LNAs

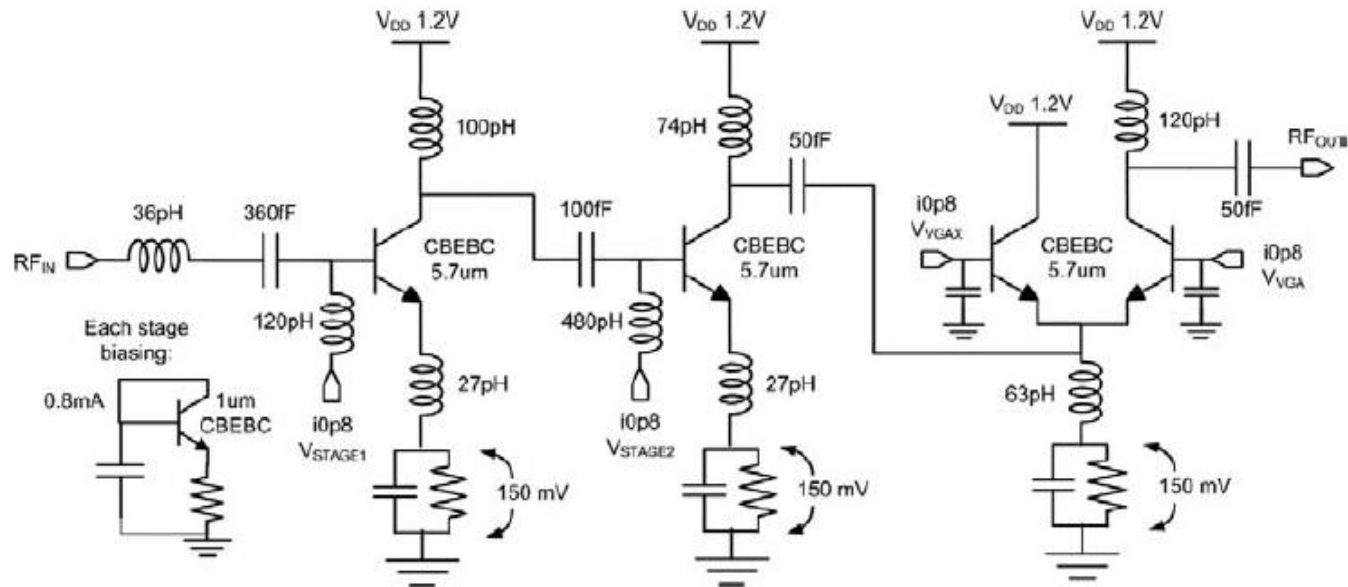

- The series bias resistor can be replaced by an inductor → part of the LNA matching network
- Emitter degeneration resistors can be used to stabilize the bias across PVT
 - Bias degeneration resistor is bypasses to eliminate its impact on LNA gain & noise

Design Example: CE Optimum Current Density

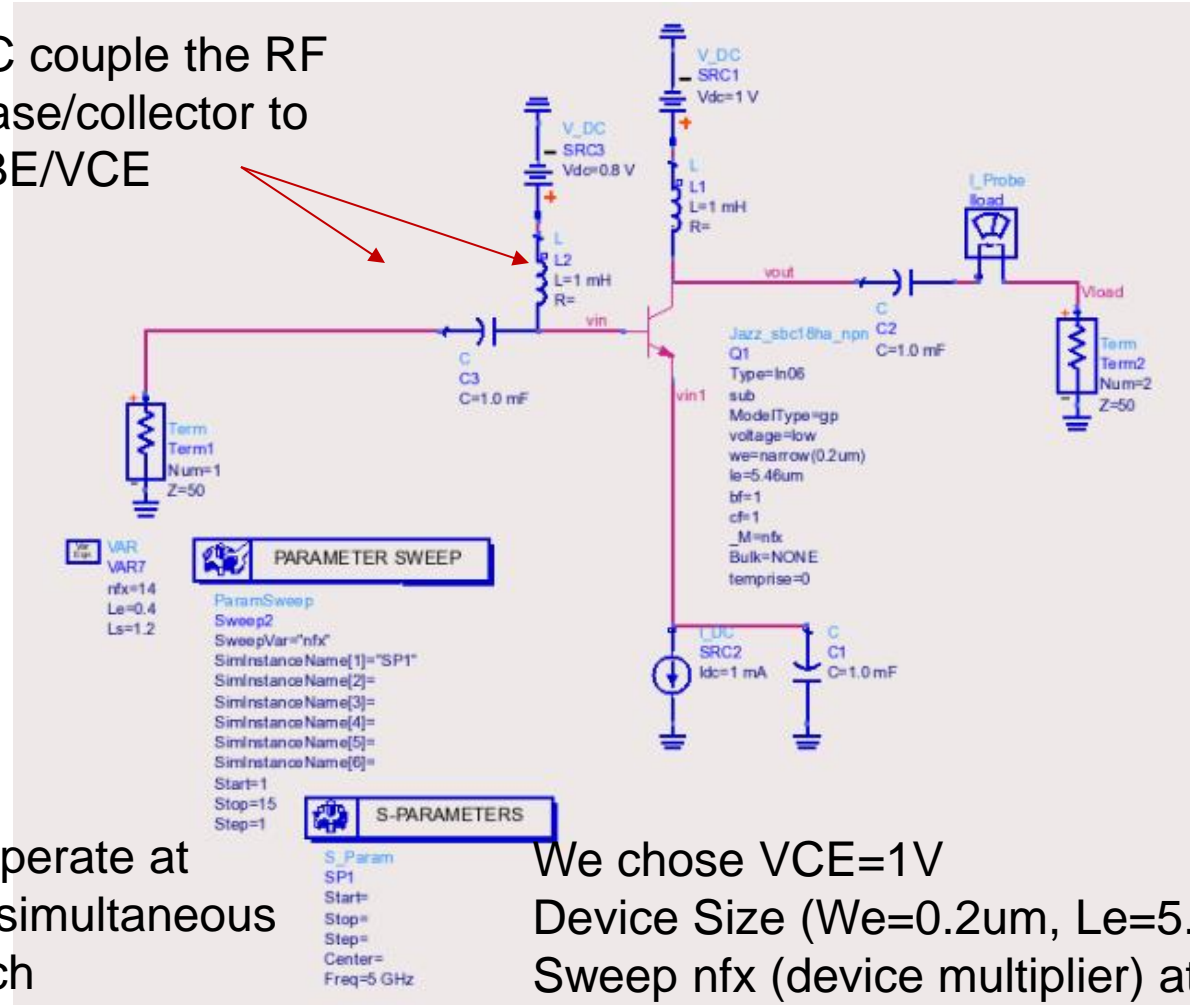Ideal bias-T used to AC couple the RF signal and Bias the base/collector to the desired VBE/VCE



- Design an LNA to operate at 5GHz and achieve simultaneous noise & power match


We chose VCE=1V
 Device Size (We=0.2um, Le=5.46um)
 Sweep nfx (device multiplier) at **1mA**

Design Example: CE Optimum Current Density

$$J_{c_opt} = I_c / \text{Device Size} = 1\text{mA} / (4 \cdot 0.2 \cdot 5.46) = 0.23\text{mA}/\mu\text{m}^2$$


Optimum number of devices in parallel = 4

 m2
freq=5.000GHz
Sopt=0.734 / 15.286
nfx=4.000000
impedance = 187.995 + j157.890



Nfx=4 for 1mA

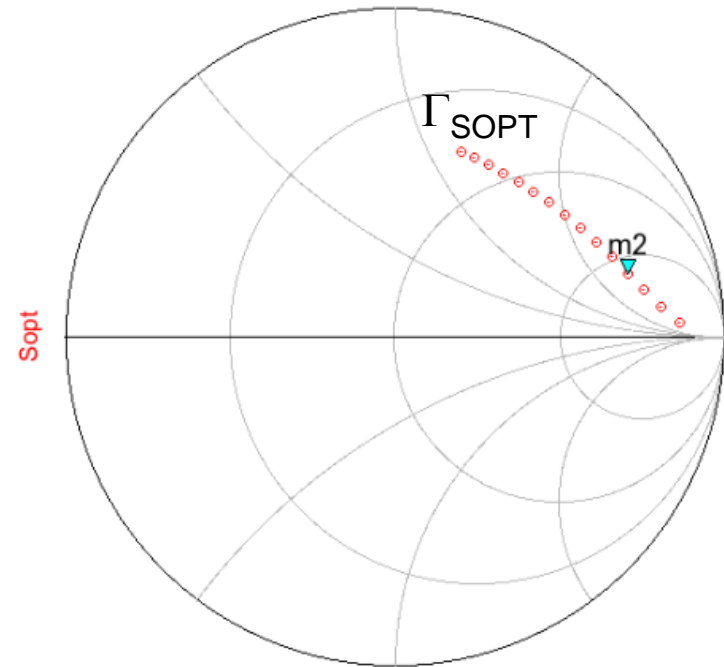Then, Nfx will equal 8 for 2mA ($I_E = nfx/4$ mA)




freq (5.000GHz to 5.000GHz)

$Z_{SOPT} = 187.9 + j157.89 \rightarrow$ far from being 50 Ohm matched




Scale the Current for $\text{Re}\{Z_{\text{SOPT}}\}=50 \text{ Ohms}$

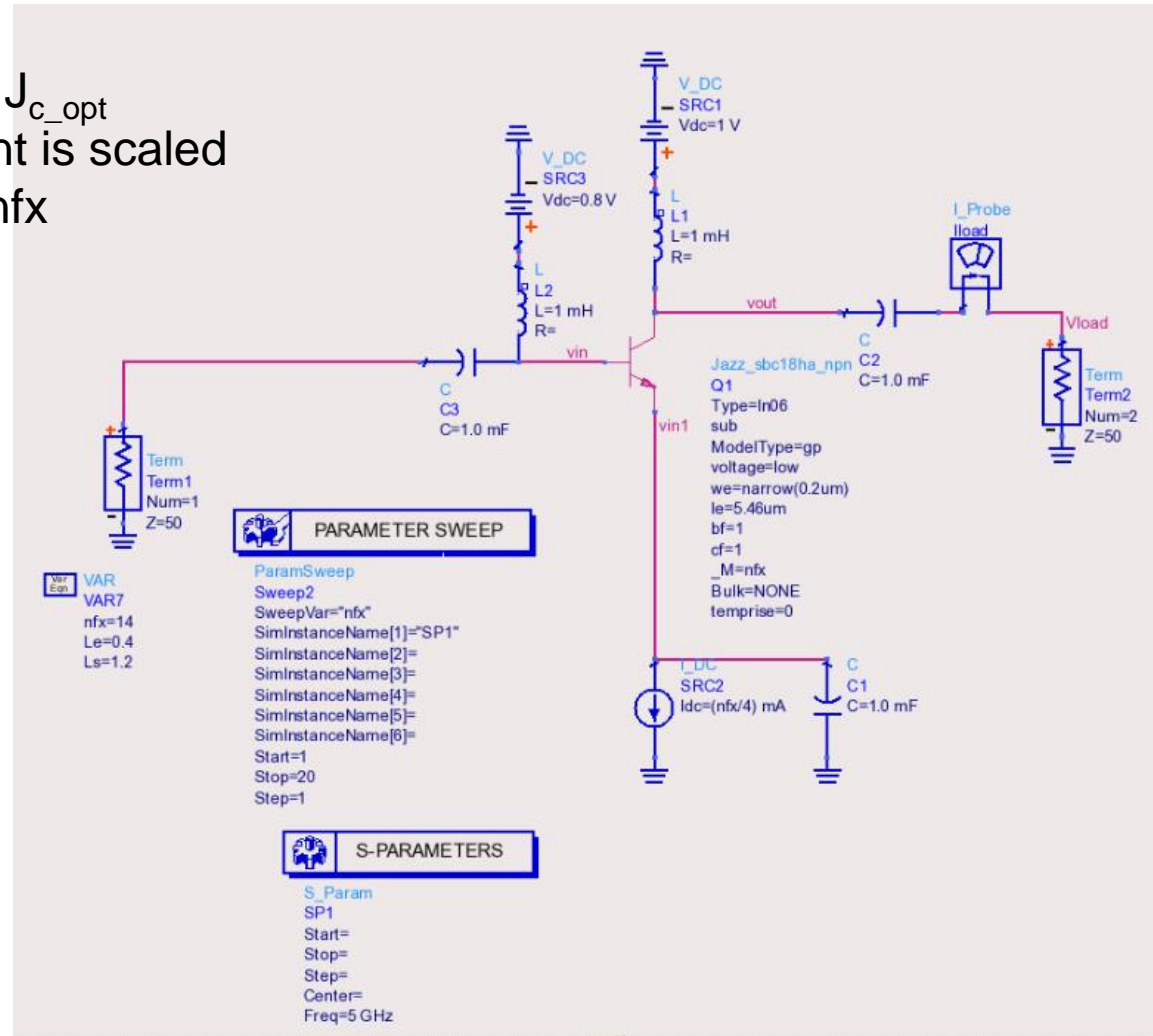- Current density fixed at: J_{c_opt}
- We swept nfx and current is scaled accordingly: $I_C = J_{c_opt} \times nfx$



Scale the Current to get $\text{re}\{Z_{\text{SOPT}}\}=50$ Ohms

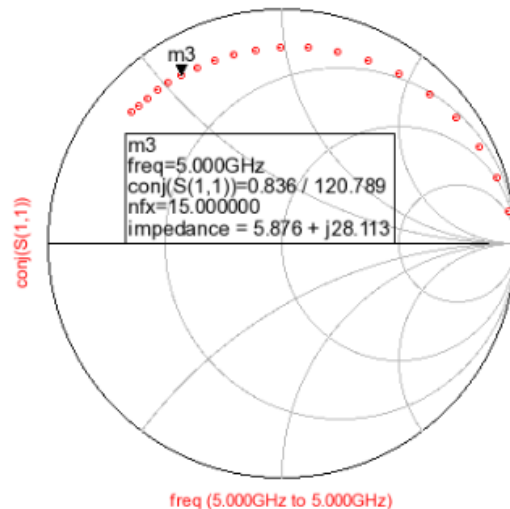  
NF_{min} doesn't change since
current density is fixed at $J_{\text{c_opt}}$



- We swept n_{fx} to get $\text{re}\{Z_{\text{opt}}\}=50$ Ohms
- However, $\text{conj}(Z_{\text{in}})=5.87+j28$ Ohms
- The device is large and hence its input impedance is small
- increase $\text{re}\{Z_{\text{in}}\}$ without deteriorating the noise match \rightarrow inductor degeneration




Inductor Degeneration L_E

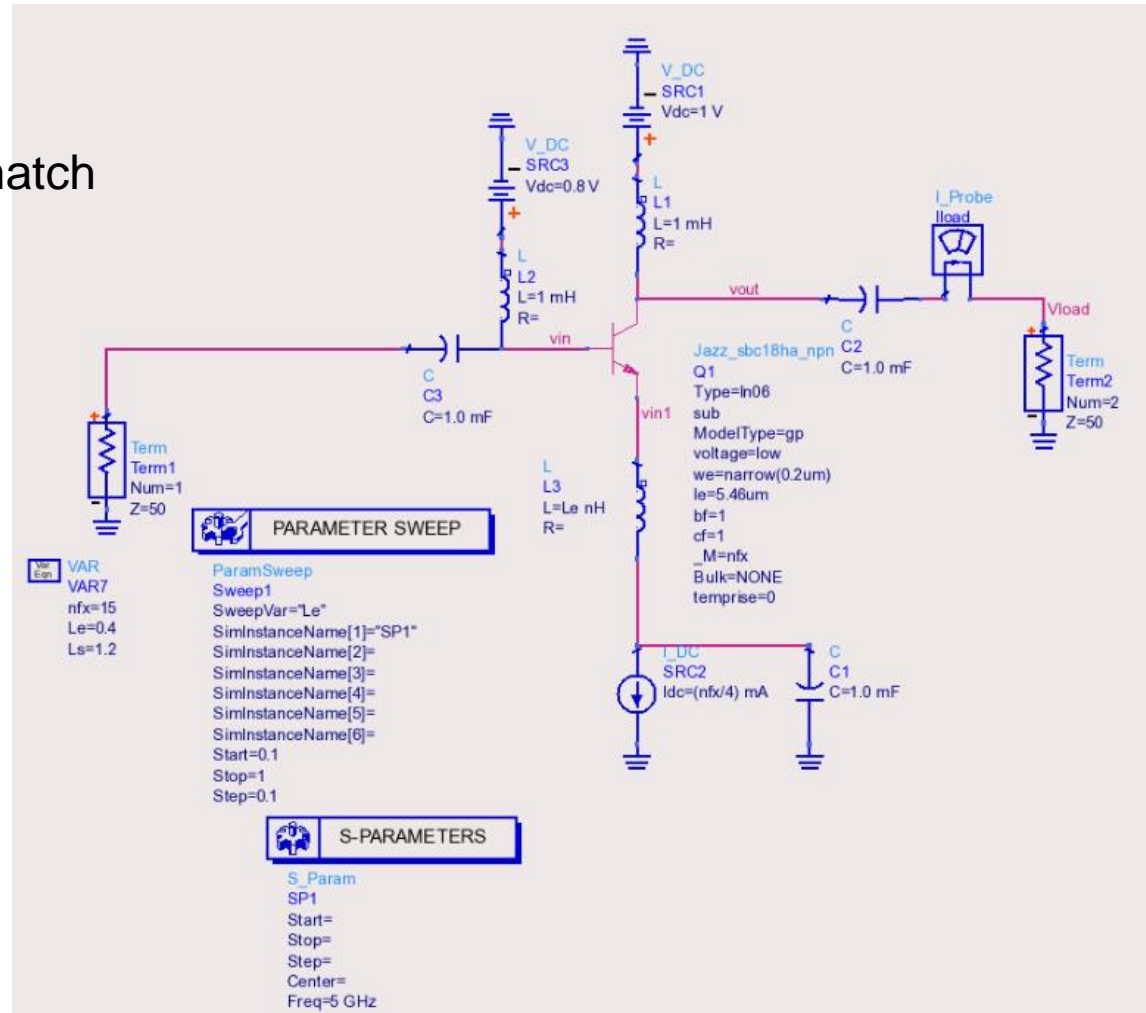Sweep L_E to match
 $\text{re}\{Z_{in}\}$ to Z_o



Inductor Degeneration L_E

   
NF_{min} doesn't change since series-series feedback using L_E doesn't affect it



- $re\{Z_{in}^*\}$ is 50 Ohms at $L_E=0.4nH$
- $re\{Z_{SOPT}\}$ doesn't change much from 50 Ohms
- There is a **small** difference between $im\{Z_{SOPT}\}$ and $im\{Z_{in}^*\}$
- Both Z_{SOPT} and Z_{in}^* require a series inductor

Series input Inductor L_B




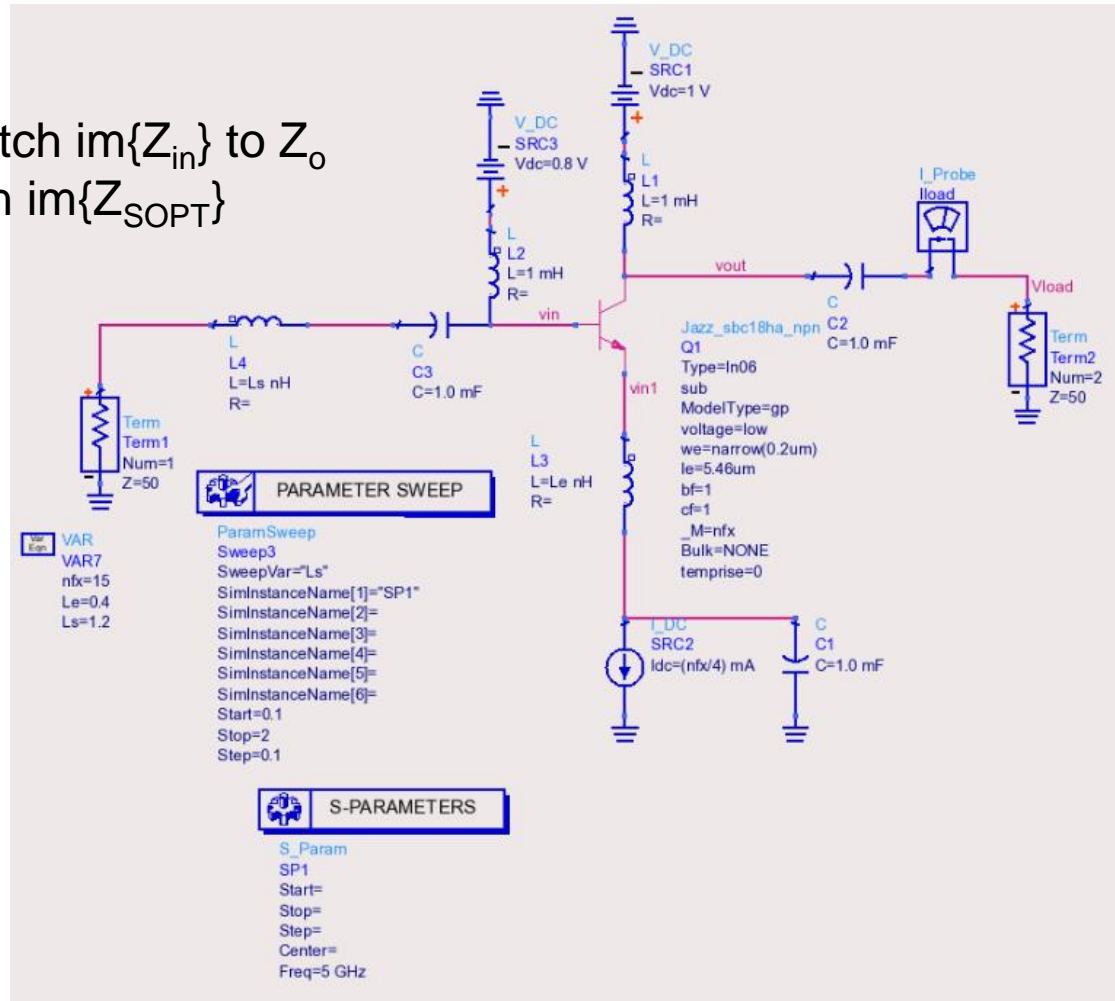
Sweep L_B to match $\text{im}\{Z_{in}\}$ to Z_0
and noise match $\text{im}\{Z_{SOPT}\}$




Series input Inductor L_B

- $L_B=1\text{nH}$ for optimum noise, $L_B=0.8\text{nH}$ for best gain match
- We can set $L_s=0.9\text{nH}$

    
After noise match
was done $NF=NF_{\min}$



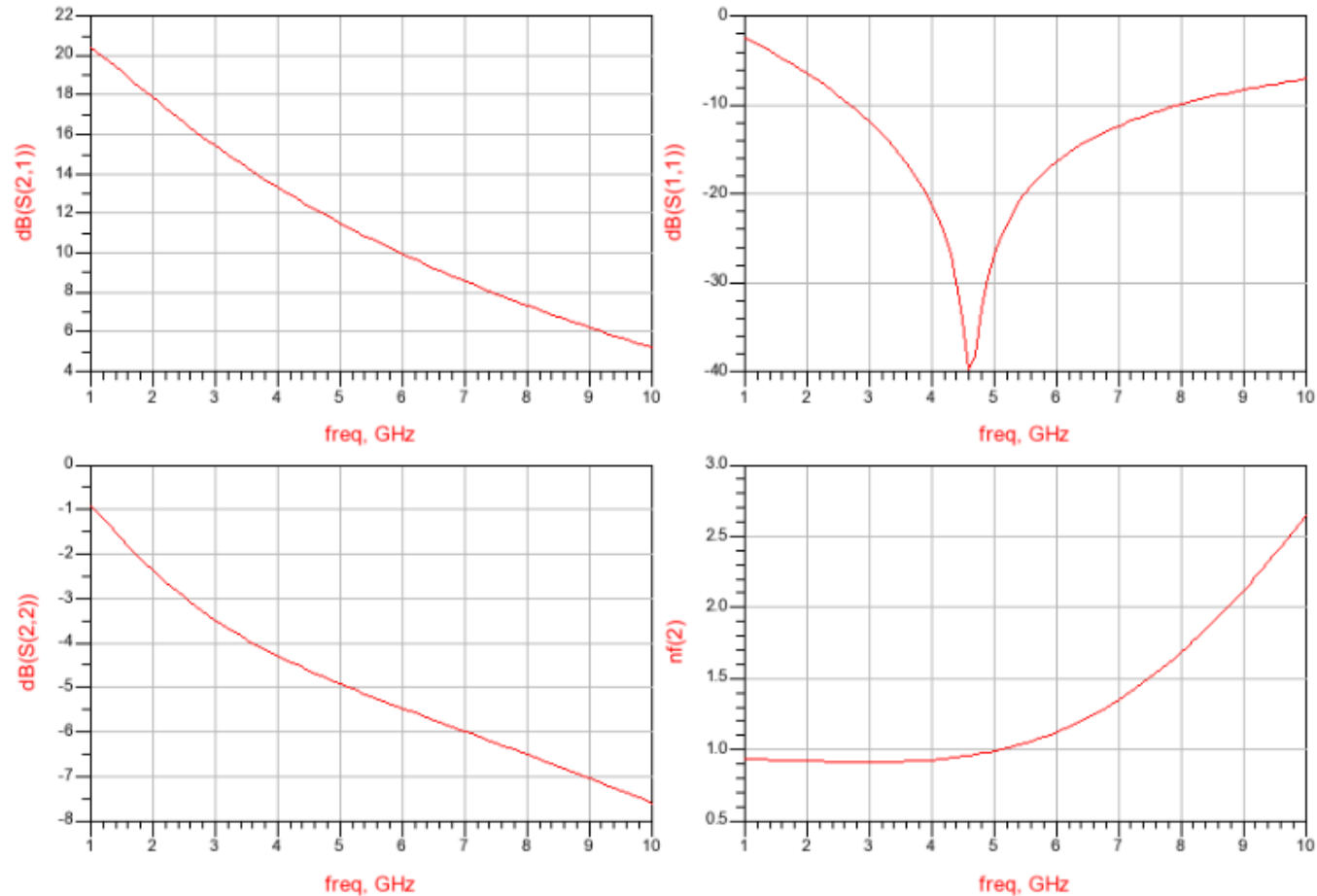
What's the total performance up till now?



Output Match: Shunt L


 


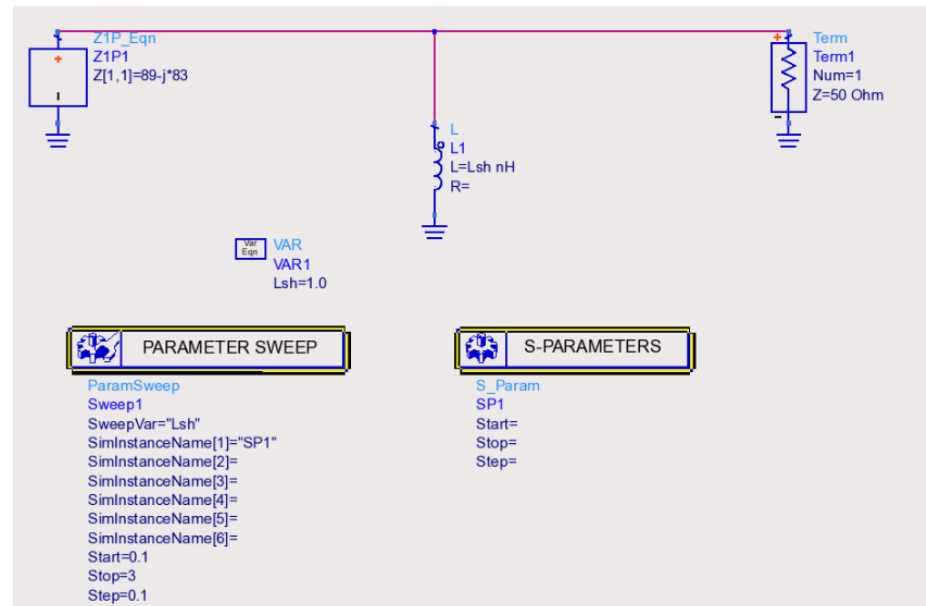- Size the shunt inductor to get the real part to Z_0




Output Match: Series C

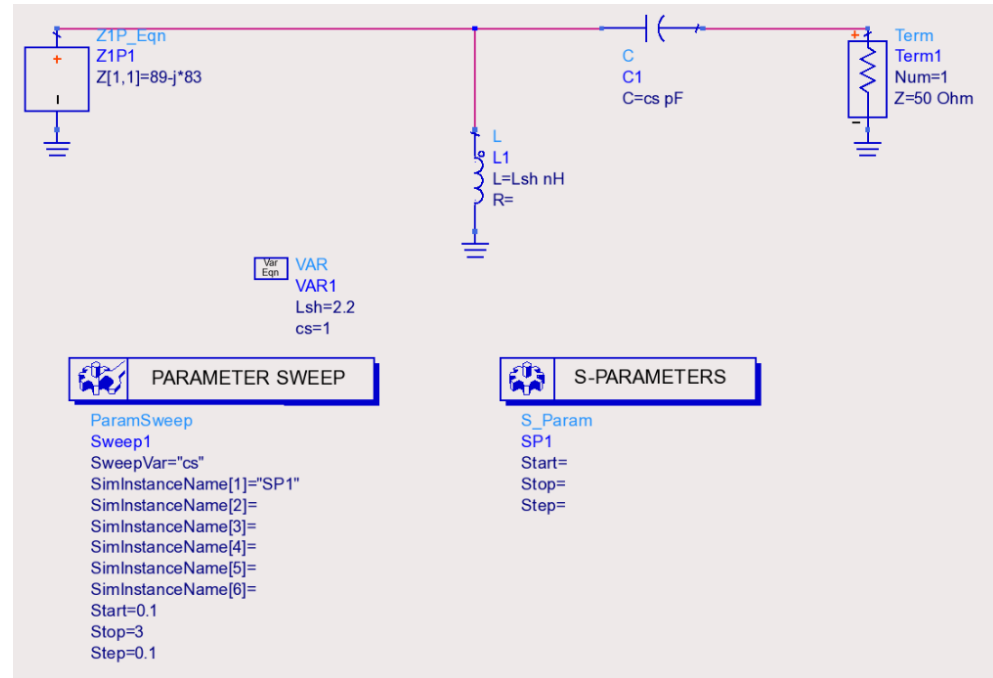 - Size the series capacitor to resonate the imaginary part




Output Matching

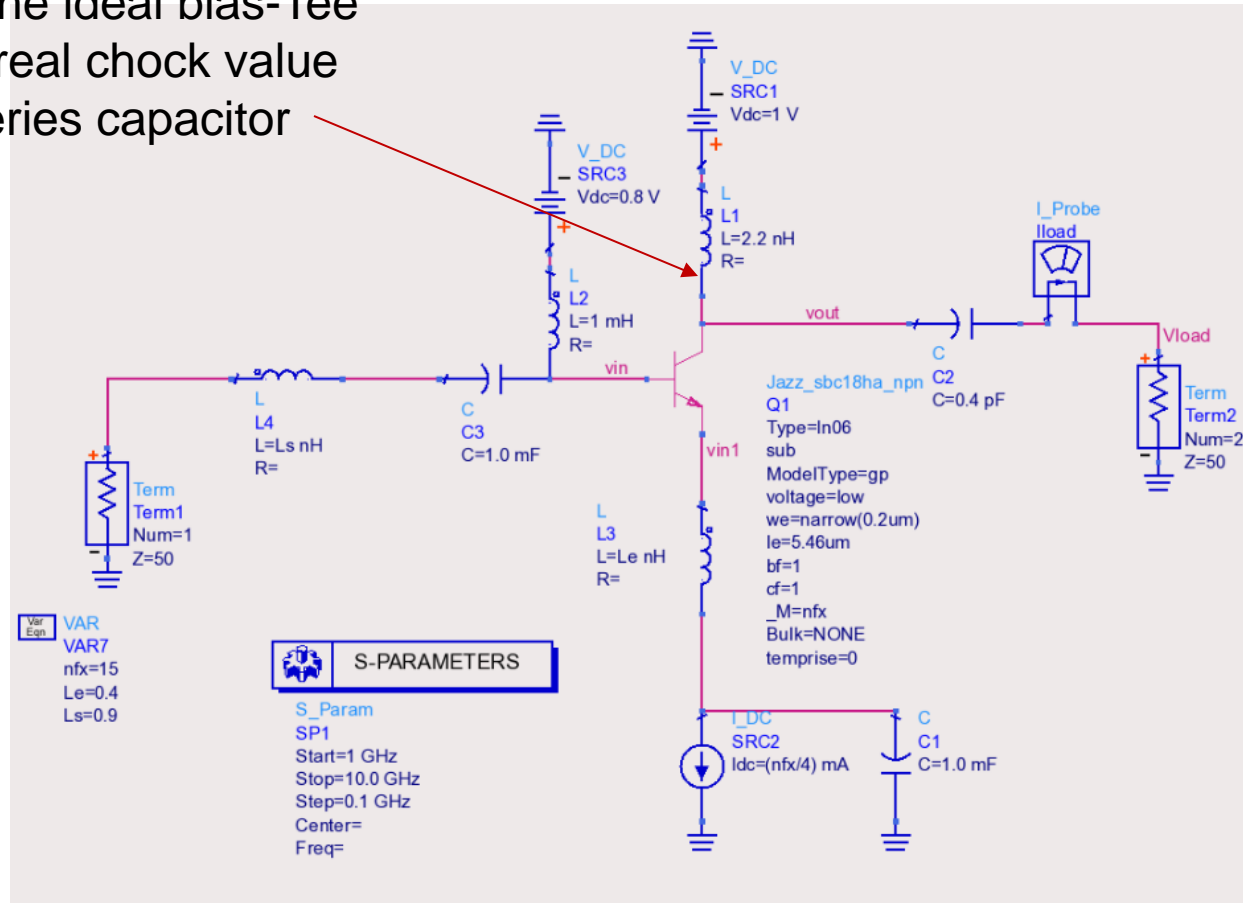Replace the ideal bias-Tee
with the real chock value
and series capacitor



Initial LNA Response




 
The output is matched but the input has been affected. Why?
Is the output really decoupled from the input?




Before and After the O/P match

Before output match

After output match

    

Optimize the design




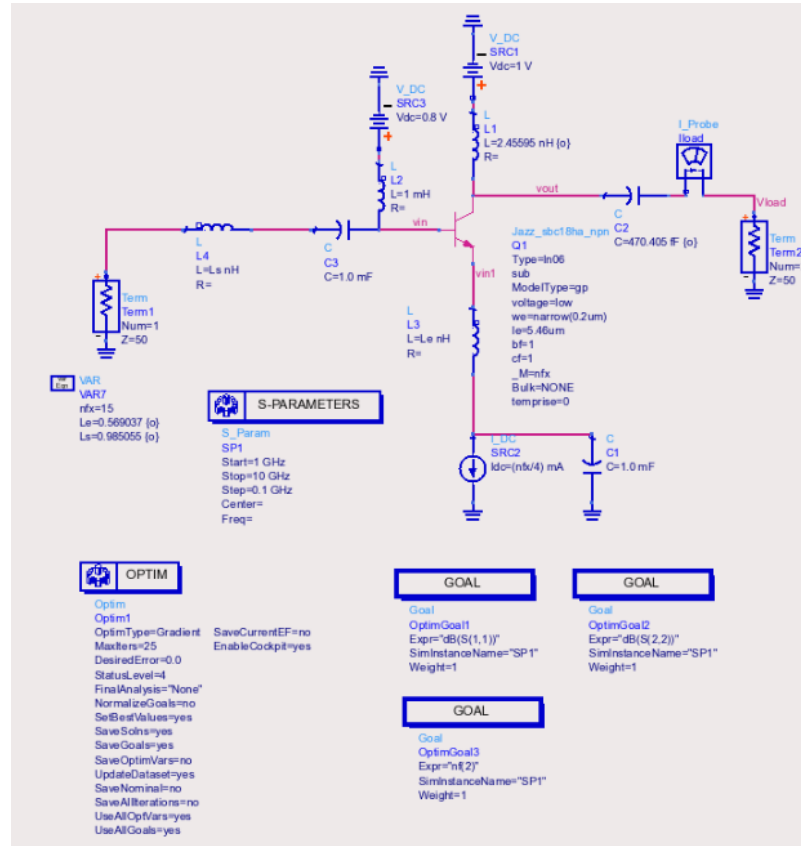


- After reaching the preliminary design ADS optimizer can be used to tweak the passive components & device current/size to improve the LNA results
- Goals can be set on NF, S_{11} , S_{22} , & S_{21}

Before and after optimization

Before optimization

After optimization

    

Design Steps for Cascoded CS with L_{M1}

1. Set the bias to the optimum NF_{MIN} current density (J_{OPT})
2. Choose the optimal W_f to minimize NF_{MIN}
3. Find the best L_M value for the cascode biased at J_{OPT} by plotting the f_T of the cascode versus L_M
4. With all devices biased at J_{OPT} , scale the number of fingers (N), and L_M to match R_{SOPT} to Z_o
5. Find L_S to match $re\{Z_{in}\}$
6. Add L_G to tune out $Im\{Z_{IN}\}$ and $Im\{Z_{SOPT}\}$
7. Add output matching network to maximize gain

